

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)
ORGANISATION OF ISLAMIC COOPERATION (OIC)
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Mid-Semester Examination

Course No.: EEE 4603

Course Title: Measurement and Instrumentation

Summer Semester, A. Y. 2021-2022

Time: 90 Minutes

Full Marks: 75

There are 2 (two) questions. Answer all 2 (two) questions. The symbols have their usual meanings. Programmable calculators are not allowed. Marks of each question and corresponding COs and POs are written in the brackets.

1. a) Explain gross and systematic errors with proper examples. 4
(CO1,
PO3)
- b) Find an expression for the gauge factor of a strain gauge. 10
(CO1,
PO3)
- c) Explain one differential arrangement of capacitive transducer and why it is advantageous over inductive transducers. 6
(CO1,
PO3)
- d) Find the expression for the quality factor of Maxwell Bridge with a proper bridge circuit and explain why it's not suitable for measuring inductance with low quality factor. 10
(CO1,
PO3)
2. a) Calculate the error from the following expression: 10
(CO2,
PO2)
- $$w = \frac{x^2 y}{z}$$
- Here $x = 10 \pm 0.2$, $y = 15 \pm 0.3$, $z = 20 \pm 0.2$.
- b) A Kelvin double bridge (Fig:1) has ratio arms $P=Q=p=q= 1000 \Omega$. The emf of the battery is 100 V and a resistance of 5Ω is included internally. The galvanometer has a resistance of 500Ω and the resistance of the link connecting the unknown resistance to the standard resistance may be neglected. The galvanometer has null deflection when $S = 0.001 \Omega$.
- i) Calculate the value of the unknown resistance.
 - ii) Calculate the current through the unknown resistance R at balanced condition.
 - iii) Calculate the deflection of the galvanometer when the unknown resistance, R, is changed by 0.1 percent from its value at balance. It has a sensitivity of 200 mm/uA.

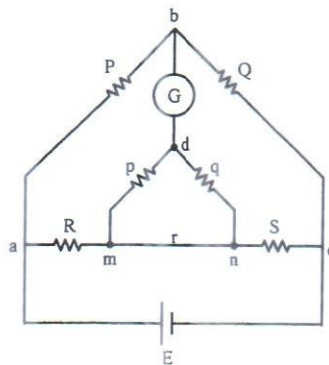


Fig: 1

- c) A Wheatstone bridge has ratio arms of $1\text{ k}\Omega$ and $100\ \Omega$. It is being used to measure an unknown resistance of $25\ \Omega$. Two galvanometers are available at hand. Galvanometer **A** has a resistance of $50\ \Omega$ and a sensitivity of $200\ \text{mm}/\mu\text{A}$ and galvanometer **B** has values of $600\ \Omega$ and $500\ \text{mm}/\mu\text{A}$. Calculate the ratio of their sensitivities and find out which one is more sensitive. 10
(CO2,
PO2)
- d) For the Maxwell's bridge (Fig: 2) $R_3=10\ \Omega$, $C=0.5\ \text{mF}$, $R_1=320\ \Omega$ and $R_2=20\ \Omega$ at balance. Calculate the Q-factor for the unknown impedance at a supply frequency of $50\ \text{Hz}$. 10
(CO2,
PO2)

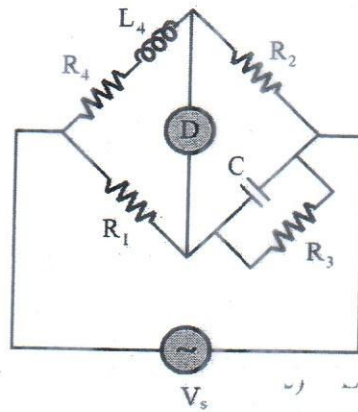


Fig: 2