

**ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)
ORGANISATION OF ISLAMIC COOPERATION (OIC)
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING**

Mid-Semester Examination

Course No.: EEE 4261

Course Title Electrical and Electronic Technology II

Summer Semester, A. Y. 2021-2022

Time: 90 Minutes

Full Marks: 75

There are **3 (three)** questions. Answer all **3 (three)** questions. The symbols have their usual meanings. Programmable calculators are not allowed. Marks of each question and corresponding COs and POs are written in the brackets. **If there is any error in the question, take suitable assumptions.**

1. a) Sketch I vs V graph for
- fig: 1a**
- and
- fig: 1b**
- .

12

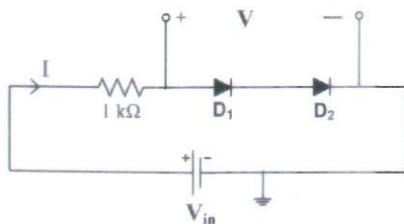


fig: 1a

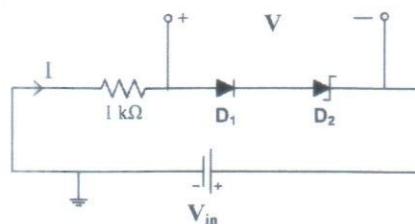


fig: 1b

CO2
PO2Here, Breakdown Voltage $V_B = -30V$ Zener Voltage, $V_Z = -5V$ For forward bias of diode, use constant voltage model with $V_f = 0.7V$ V_{in} is varied from -50V to 50V.

- b) Sketch output graph
- V_{out}
- for
- fig: 2d**
- for the voltage profiles in
- fig: 2a, 2b**
- and
- 2c**
- . Consider ideal voltage diode model for all diodes.

13

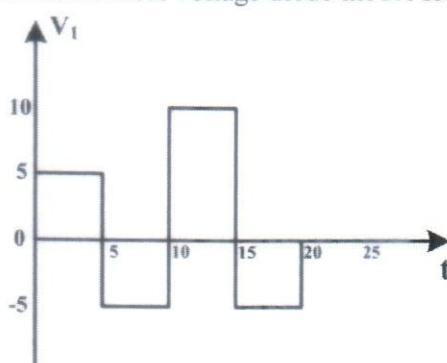


fig: 2a

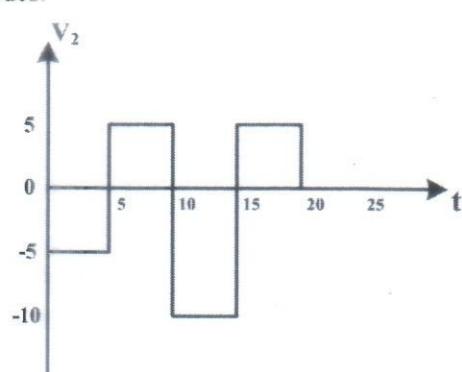


fig: 2b

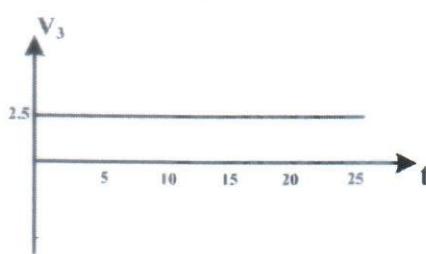
CO2
PO2

fig: 2c

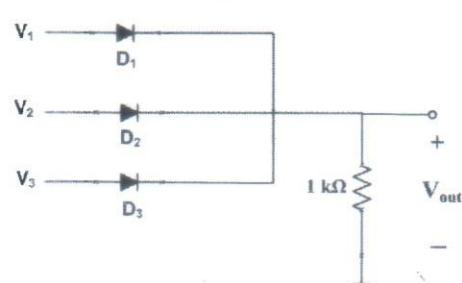


fig: 2d

2.

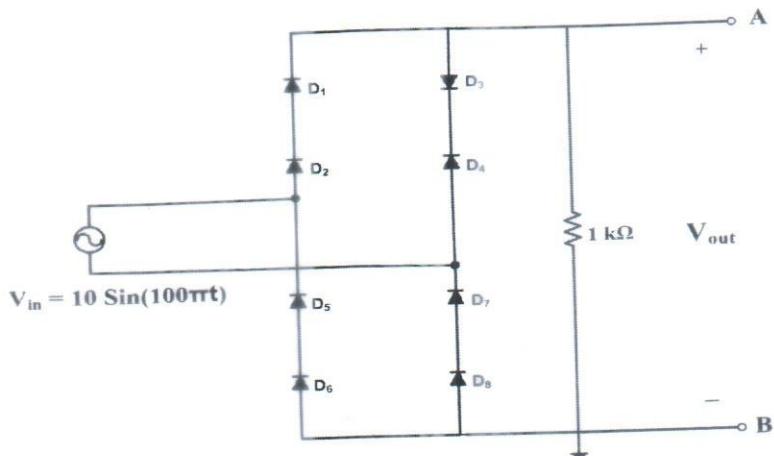


fig: 3

In **fig:3**, Breakdown Voltage $V_B = -30V$
For forward bias of diode, use constant voltage model with $V_f = 0.7V$

- a) Sketch V_{out} . 5
CO2
PO2
 - b) Sketch V_{out} when $200 \mu F$ capacitor is connected between node A and B. 10
CO2
PO2
 - c) Sketch V_{out} if D_3 is replaced with a zener diode of $V_Z = -5V$. The anode and cathode of zener diode will be connected to the nodes same as the anode and cathode of D_3 . 10
CO2
PO2
3. a) Analyze the circuit in **fig.4** to determine the voltages at all nodes and the currents in all branches. Assume $\beta = 100$. 15
CO2
PO2

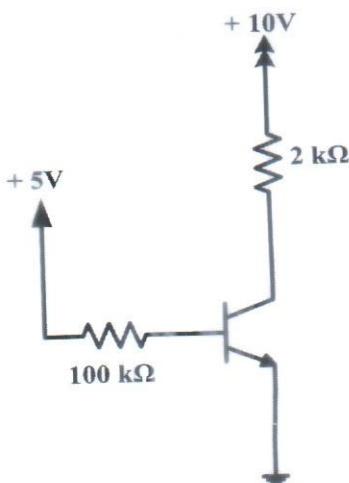


fig: 4

- b) Describe different operating modes of BJT along with proper circuit configurations. 10
CO1
PO1