

3. a) Simplify the following Boolean expressions into a POS format following *Quine-McCluskey* method and implement those expressions with at most two-level NOR gates. 10
(CO4)

$$F(A, B, C, D) = ABC + A'B'CD' + A'BC'D$$
(PO1)

$$d(A, B, C, D) = B'D + A'BD' + AB'D'$$
- b) Differentiate between: 5
- i. Boolean algebra and ordinary algebra (CO3)
 - ii. Canonical form and Standard form of Boolean function (PO2)
 - iii. Flat and dual line IC
 - iv. Combinational and Sequential circuit.
 - v. Carry and Borrow in MSB
- c) Define '*number*' and '*algebra*' under any mathematical system with required constraints. 5
(CO1)
(PO1)
- d) Draw a full-adder and a full-subtractor using corresponding half-adder and half-subtractor respectively. 5
(CO2)
(PO2)