

B.Sc. in CSE, 2nd Semester

Date: 08 May 2023

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)

ORGANISATION OF ISLAMIC COOPERATION (OIC)

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Semester Final Examination

Summer Semester: 2021 - 2022

Course No.: PHY 4241

Full Marks: 150

Course Title: Physics II

Time: 3 hrs.

There are **06 (six)** questions. Answer all **06 (six)** questions. The symbols have their usual meanings.
 Marks of each question and corresponding CO and PO are written in brackets.

1. i. Find I_s in the circuit in Fig. 1(a). Here, $V_0 = 8\angle 30^\circ$.

8

(CO2)

(PO1, PO2)

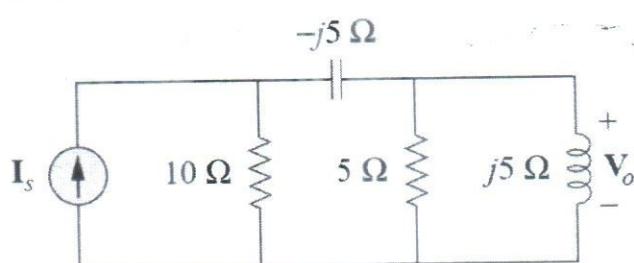


Fig. 1(a)

- ii. Find V_s in the circuit in Fig. 1(b). Here, $I_0 = 2\angle 0^\circ$.

8

(CO2)

(PO1, PO2)

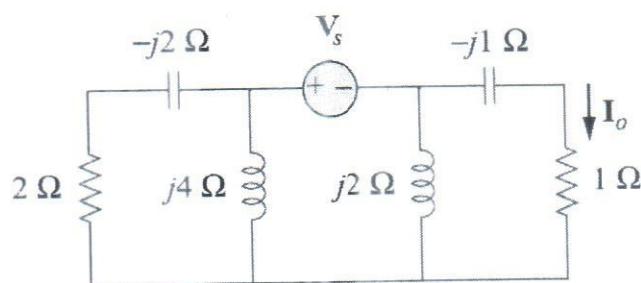


Fig. 1(b)

- iii. For the circuit in Fig. 1(c), find Z_{eq} .

9

(CO2)

(PO1, PO2)

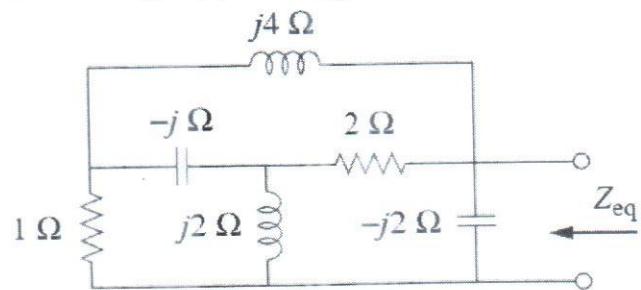


Fig. 1(c)

2. i. Find V_0 for the circuit in Fig. 2(a) using Nodal analysis.

12
(CO2)
(PO1, PO2)

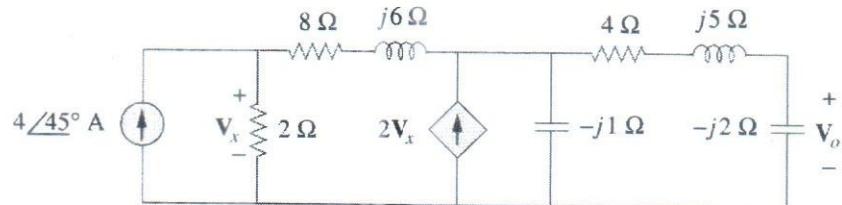


Fig. 2(a)

- ii. Find I_0 for the circuit in Fig. 2(b) using Mesh analysis.

13
(CO2)
(PO1, PO2)

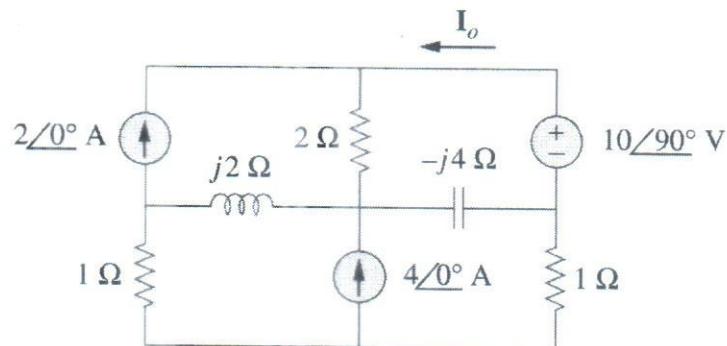


Fig. 2(b)

3. i. Find i_0 for the circuit in Fig. 3(a).

12
(CO2)
(PO1, PO2)

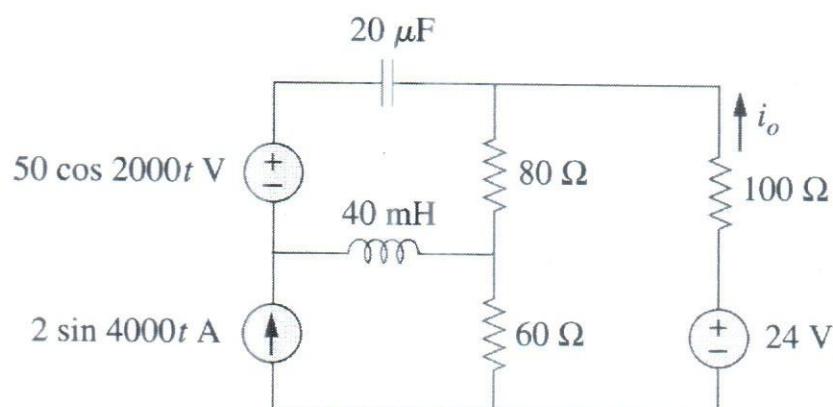


Fig. 3(a)

- ii. Find the Thevenin equivalent at terminal a-b in the circuit of Fig. 3(b).

13

(CO2)

(PO1, PO2)

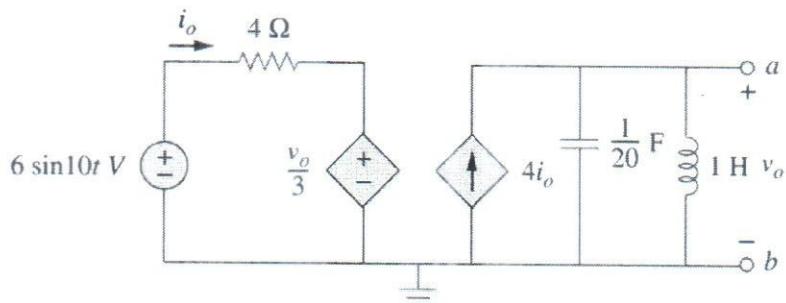


Fig. 3(b)

4. i. Find C_{eq} for the circuit in Fig. 4(a). All capacitors are $4 \mu\text{F}$.

8

(CO2)

(PO1, PO2)

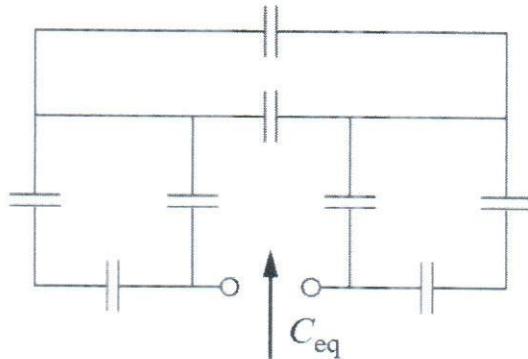


Fig. 4(a)

- ii. Find voltages across the capacitors for the circuit in Fig. 4(b).

8

(CO2)

(PO1, PO2)

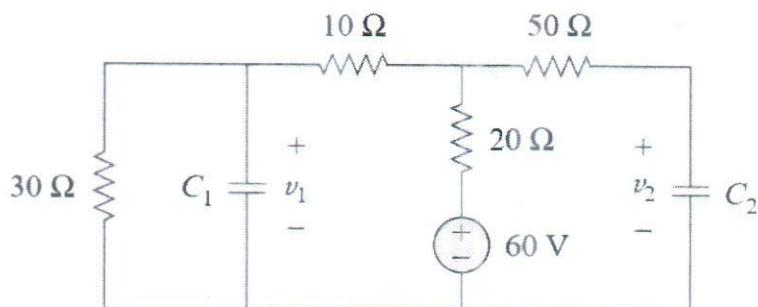


Fig. 4(b)

- iii. For the circuit in Fig. 4(c), find L_{eq} , $i_1(t)$, $i_2(t)$, $v_o(t)$, and energy stored in the 20-mH inductor at 1s. Here, $i_s(t) = 3e^{-t}mA$.

9
(CO2)
(PO1, PO2)

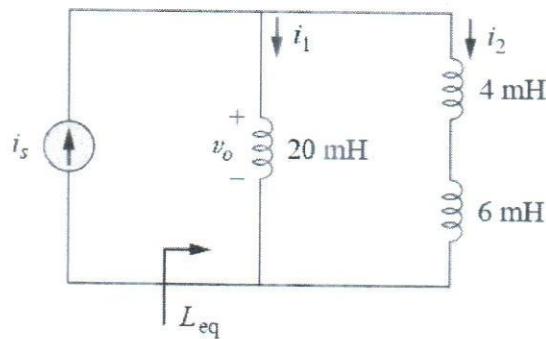


Fig. 4(c)

- 5.** i. Determine the resonant frequency for the circuit in Fig. 5(a).

8
(CO2)
(PO1, PO2)

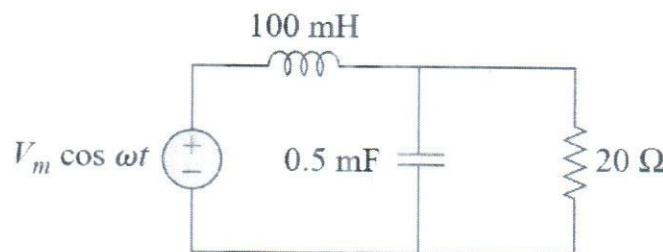


Fig. 5(a)

- ii. Determine ω_0 , Q , and B for the circuit in Fig. 5(b). Here, $v_o = 20 \cos \omega t$.

8
(CO2)
(PO1, PO2)

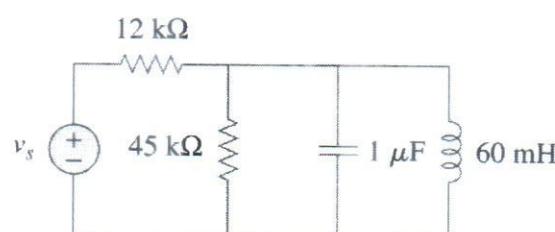


Fig. 5(b)

- iii. Find the transfer function for the circuit in Fig. 5(c) and determine what type of filter it represents.

9
(CO2)
(PO1, PO2)

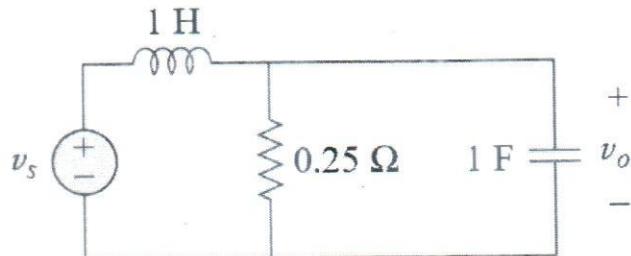


Fig. 5(c)

6. i. Design a BPF using a series RLC network that has a lower cut-off frequency of 20.1 KHz and an upper cut-off frequency of 20.3 KHz. Take $R=20\text{K}\Omega$. Determine L, C and Q.

8
(CO2)
(PO1, PO2)

- ii. Determine the load impedance that maximizes the average power drawn from the circuit in Fig. 6(b). Calculate the maximum average power.

8
(CO2)
(PO1, PO2)

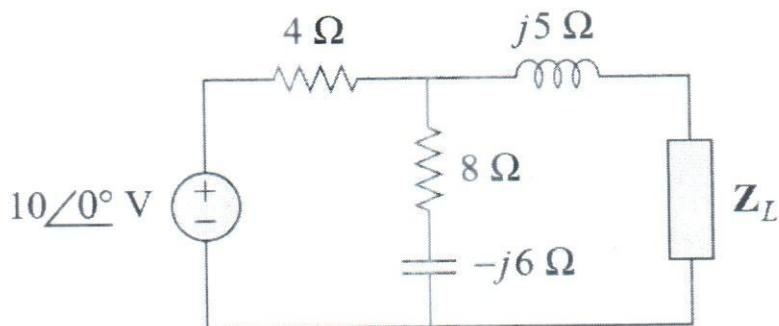


Fig. 6(b)

- iii. Explain the concept of power flow in ac circuit and the significance of power factor. Draw the power triangle and explain complex power, real power and reactive power.

9
(CO2)
(PO1, PO2)