

B. Sc. in EEE, 4<sup>th</sup> Sem.  
DTE, 2<sup>nd</sup> Sem.

Date: 12 May, 2023  
Time: 10:00 am–1:00 pm

**ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)**  
ORGANISATION OF ISLAMIC COOPERATION (OIC)  
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Semester Final Examination  
Course Number: EEE 4401/ EEE 4495  
Course Title: Power System II

Summer Semester : 2021 - 2022  
Time : 3 Hours  
Full Marks: 150

There are 06 (six) questions. Answer all 06 (six) questions. The symbol(s) have their usual meanings. Marks of each question and corresponding CO's and PO's are written in the brackets. Assume reasonable value for any missing data.

1. a) A generator having a solidly grounded neutral and rated 50 MVA, 30 kV has positive-, negative-, and zero-sequence reactances of 25, 15, and 5 percent, respectively. Find out what reactance must be placed in the generator neutral to limit the fault current for a bolted line-to-ground fault to that for a bolted three-phase fault. (10) (CO1) (PO1)
- b) Three 15 MVA, 30 kV synchronous generators A, B, and C are connected via three reactors to a common bus bar, as shown in Fig. 1(b). The neutrals of generators A and B are solidly grounded, and the neutral of generator C is grounded through a reactor of 2.0 Ω. The generator data and the reactance of the reactors are tabulated below. (15) (CO2) (PO2)

Item	$X^1$	$X^2$	$X^0$
$G_A$	0.25 pu	0.155 pu	0.056 pu
$G_B$	0.20 pu	0.155 pu	0.056 pu
$G_C$	0.20 pu	0.155 pu	0.060 pu
Reactor	6.0 Ω	6.0 Ω	6.0 Ω

A line-to-ground fault occurs on phase a of the common bus bar. Neglect pre-fault currents and assume generators are operating at their rated voltage. Determine the fault current in phase a.

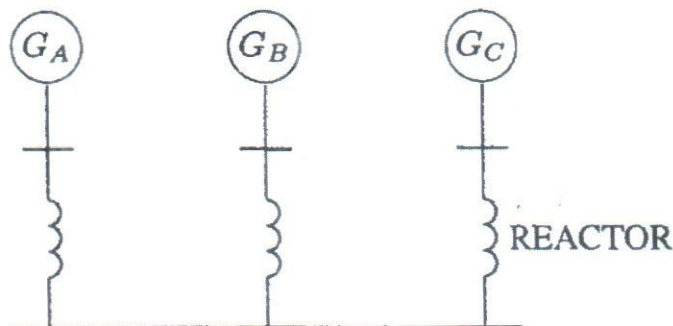


Fig. 1(b)

2. One line diagram of a simple three bus power system with generation at bus 1 is shown in Fig. 2. The voltage at bus 1 is  $V_1 = 1.05 \angle 0^\circ$  per unit. Voltage magnitude of bus 3 is fixed at 1.04 pu with a real power generation of 200 MW. A load consisting of 400 MW and 250 MVAR is taken from bus 2. Line impedances are marked in per unit on a 100 MVA base. Sketch the power flow diagram by the *Gauss-Seidel method* including line flows and line losses. Perform *two* iterations. (25) (CO2) (PO2)

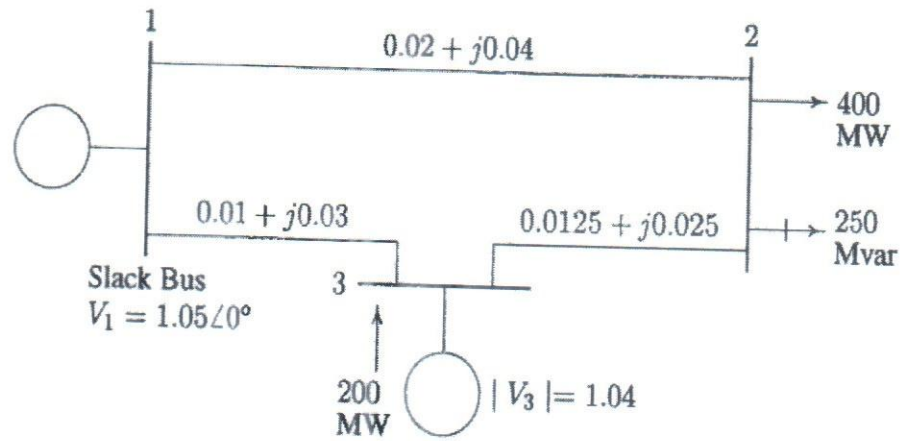


Fig. 2

3. The one line diagram of a simple three bus power system is shown in Fig. 3. Each generator is represented by an emf behind the subtransient reactance. All impedances are expressed in per unit on a common MVA base. All resistances and shunt capacitances are neglected. The generators are operating on no load at their rated voltage with their emfs in phase. A *three-phase fault* occurs at bus 3 through a fault impedance of  $Z_f = j0.19$  per unit. (13+ 12) (CO3) (PO3)
- (i) Design the system using *Thevenin's theorem* by calculating the impedance to the point of fault and the fault current in per unit.
- (ii) Also determine the bus voltages and line currents during fault.

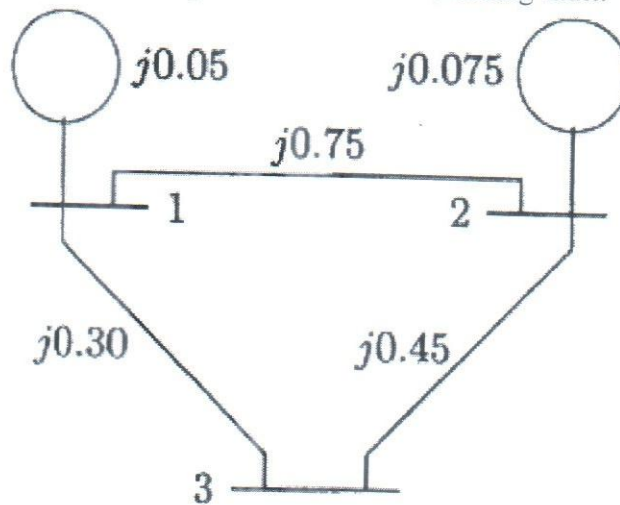


Fig. 3

4. The per unit bus impedance matrix for the power system shown in Fig. 4 is given by following  $Z_{bus}$ . A *three-phase fault* occurs at bus 4 through a fault impedance of  $Z_f = j0.0025$  per unit. Design the system using the *bus impedance matrix method* by computing the following(s):
- i) fault current, ii) bus voltages, and iii) short circuit currents in the lines during fault.

$$Z_{bus} = j \begin{bmatrix} 0.150 & 0.075 & 0.140 & 0.135 \\ 0.075 & 0.1875 & 0.090 & 0.0975 \\ 0.140 & 0.090 & 0.2533 & 0.210 \\ 0.135 & 0.0975 & 0.210 & 0.2475 \end{bmatrix}$$

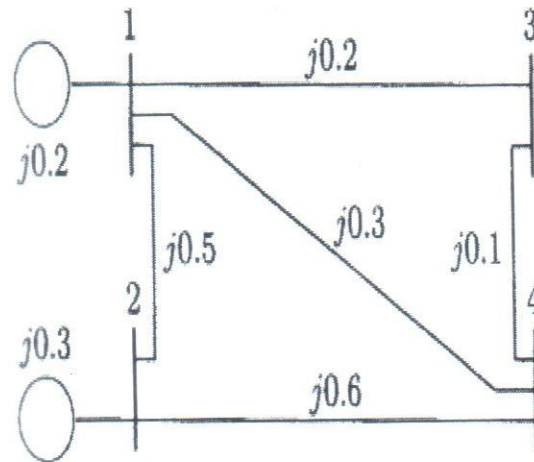


Fig. 4

5. The one line diagram of a three phase power system is as shown in Fig. 5. The transformer reactance is 20 percent on a base of 100 MVA, 23/115 kV and the line impedance is  $Z = j66.125 \Omega$ . The load at bus 2 is  $S_2 = 184.8 \text{ MW} + j6.6 \text{ Mvar}$ , and at bus 3 is  $S_3 = 0 \text{ MW} + j20 \text{ Mvar}$ . It is required to hold the voltage at bus 3 at  $115 \angle 0^\circ$  kV. Determine the per unit as well as actual values of the following(s):
- i) voltage at bus 2 and  
ii) voltage at bus 1.

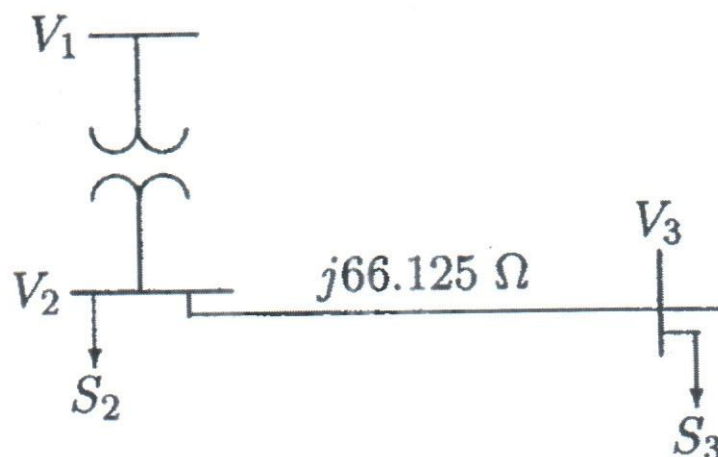


Fig. 5

6. a) In the three phase system shown in Fig. 6(a), phase a is on no load and phases b and c are short circuited to ground. The following currents are given:  $I_b = 91.65 \angle 160.9^\circ$  and  $I_n = 60.00 \angle 90^\circ$ . Sketch the symmetrical components of current for phase a,  $I_a^{(0)}$ ,  $I_a^{(1)}$ , and  $I_a^{(2)}$  using *Fortescue's theorem*. (12) (CO1) (PO1)

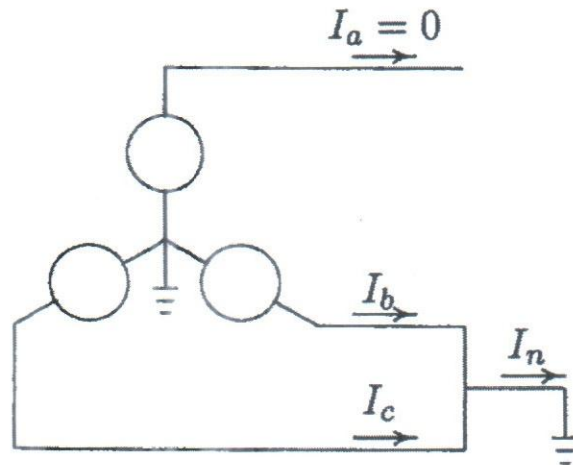


Fig. 6(a)

- b) Using the method of *building algorithm*, find the bus impedance matrix,  $Z_{bus}$  for the network shown in Fig. 6(b). (13) (CO2) (PO2)

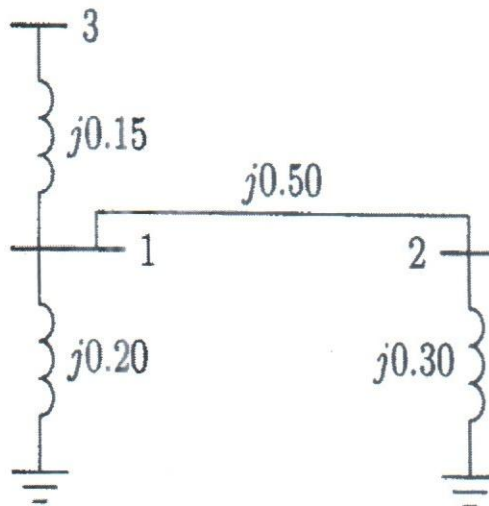


Fig. 6(b)