

7

B.Sc. in EEE, 3rd Semester  
DTE, 1st Semester

Date: October 04, 2023  
Time: 2:30 pm to 4:00 pm

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)  
ORGANISATION OF ISLAMIC COOPERATION (OIC)  
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Mid Semester Examination  
Course No.: EEE 4301 / EEE 4395  
Course Title: Electrical Power Transmission and Distribution

Winter Semester, A. Y. 2022-2023  
Time: 1.5 Hours  
Full Marks: 75

There are 3 (three) questions. Answer all 3 (three) questions. The symbols have their usual meanings. Programmable calculators are not allowed. Marks of each question and corresponding COs and POs are written in the brackets.

- 
1. a) Discuss the relative merits and demerits of underground and overhead systems. Explain briefly the following systems of distribution : [6+3+3]  
(CO1,  
PO1)
    - (i) Radial system, and
    - (ii) Ring main system.
  
  - b) A 3-phase ring distributor ABCD fed at A at 11 kV supplies balanced loads of 40 A at 0.8 p.f. lagging at B, 50 A at 0.707 p.f. lagging at C and 30 A at 0.8 p.f. lagging at D, the load currents are referred to as the supply voltage at A. The impedances per phase of the various sections are:  
Section AB =  $(1 + j 2) \Omega$ ; Section BC =  $(2 + j 3) \Omega$   
Section CD =  $(1 + j 1) \Omega$ ; Section DA =  $(3 + j 4) \Omega$ .  
Calculate the currents in various sections and station bus-bar voltages at B, C, and D. [7+6]  
(CO2,  
PO2)
  
  2. a) State the necessity of using isolators on both sides of the circuit breaker. Why do we use C.T. in the relay circuit? Discuss the different types of bus-bar arrangements used in sub-stations. Illustrate your answer with suitable diagrams. [3+3+9]  
(CO1,  
PO1)
  
  - b) In a 3-phase, 4-wire, 400/230 V system, a lamp of 100 watts is connected to one phase and neutral, and a lamp of 150 watts is connected to the second phase and neutral. If the neutral wire is disconnected accidentally, determine the voltage across each lamp. [5+5]  
(CO2,  
PO2)
  
  3. a) Give the comparison of outdoor and indoor sub-stations. Sketch the key diagram of a typical 11 kV/400 V indoor sub-station. [6+5]  
(CO1,  
PO1)
  
  - b) A 2-wire radial d.c. distributor AB, 900 meters long is fed at A at 400 V, and loads of 50 A, 100 A, and 150 A are tapped off from C, D, and E which are at a distance of 200 m, 500 m, and 800 m from point A respectively. The distributor is also loaded uniformly at the rate of 0.5 A/m. If the resistance of the distributor per meter (go and return) is  $0.0001 \Omega$ , calculate the voltage for the following locations:  
    - (i) at point B, and
    - (ii) at point D.[7+7]  
(CO2,  
PO2)