



ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)
ORGANISATION OF ISLAMIC COOPERATION (OIC)
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Mid-Semester Examination
Course No.: EEE 4303
Course Title: Electronics II

Winter Semester, A.Y. 2022-2023
Time: 90 Minutes
Full Marks: 75

There are 3 (three) questions. Answer all 3 (three) questions. The symbols have their usual meanings. Programmable calculators are not allowed. Marks of each question and corresponding COs and POs are written in the brackets.

- 1. a) Formulate the expression of output voltage for a non-inverting summing amplifier in case of three input voltages. (12.5) (CO1) (PO1)
- b) Determine the equation of the closed-loop voltage gain, A_v , of the T-feedback inverting amplifier shown in Fig. 1(b). (12.5) (CO2) (PO2)

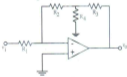


Fig. 1(b)

- 2. a) Sketch the Bode plots (magnitude & phase) for the transfer function, (12.5) (CO1) (PO1)
- $$H(\omega) = \frac{8(j\omega+2)}{j\omega(j\omega+10)}$$
- b) Explain the Bode plot in Fig. 2(b) and find the transfer function $H(\omega)$. (12.5) (CO2) (PO2)

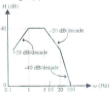


Fig. 2(b)

- 3. a) sketch the circuit diagram of a unity gain amplifier and a precision half-wave rectifier circuit with its voltage transfer characteristics using op-amp. (12.5) (CO1) (PO1)
- b) Design a two-pole high-pass Butterworth active filter with a cutoff frequency at $f_{3dB} = 25$ kHz and a unity gain magnitude at high frequency. Also determine the magnitude (in dB) of the gain at $f = 25$ kHz. (12.5) (CO2) (PO2)