

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)
ORGANISATION OF ISLAMIC COOPERATION (OIC)
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Mid-Semester Examination

Course No.: EEE 4307

Course Title: Digital Electronics

Winter Semester, A. Y. 2022-2023

Time: 90 Minutes

Full Marks: 75

There are 3 (**three**) questions. Answer all 3 (**three**) questions. The symbols have their usual meanings. Programmable calculators are not allowed. Marks of each question and corresponding COs and POs are written in the brackets.

-
1. a) A **Senary numeral system** (also known as base-6 or heximal) has six as its base and 0, 1, 2, L, M and N as its independent digits. 12
(CO1,
PO1)
- (i) Determine the decimal equivalent of $(12NLM.M2)_6$.
- (ii) Show the subtraction operation, $A-B$, using $(r-1)$'s complement where $A = (ML2N)_6$ and $B = (N21)_6$.
- b) Using Boolean algebraic manipulation, show that, 6
(CO2,
PO1)
- $$A\bar{B}C + \bar{A}BC + ABC + A\bar{B}\bar{C} = A + BC.$$
- c) Show that the dual of the exclusive-OR is equal to its complement. 5
(CO2,
PO1)
2. a) Find the simplified expression of the following function using K-Map and implement the simplified function using two level NOR-gates. 7
(CO2,
PO2)
- $$F(A, B, C, D) = A\bar{C} + \bar{B}D + \bar{A}CD + ABCD$$
- b) Design a "full-adder". Hence, Construct an eight-bit parallel adder using eight "full-adder" circuits. What is the draw-back of using this parallel adder? Design the 8-bit parallel adder using *look-ahead* carry generator. Show all the necessary Boolean expressions and logic diagrams. 15
(CO3,
PO2)
3. a) An 8×1 multiplexer has inputs A, B and C connected to the selection inputs S_2, S_1 and S_0 respectively. The data inputs, I_0 through I_7 are as follows: 10
(CO2,
PO2)
- $$I_1 = I_2 = I_7 = 0;$$
- $$I_3 = I_5 = 1,$$
- $$I_0 = I_4 = D; \text{ and } I_6 = D'.$$

Determine the Boolean function that the multiplexer implements.

- b) For the Senary numeral system mentioned in question 1(a), design a Binary Coded Senary (BCS) adder where the adder will take two BCS numbers, $A = A_2A_1A_0$ and $B = B_2B_1B_0$, and the results are to be shown in BCS form. 20
(CO3,
PO2)
- (Hint: The BCS form of a Senary number $(L2N)_6$ is 011 010 101)