

Name of the Program: B. Sc. in CEE  
Semester: 3<sup>rd</sup>

Date: 06 October, 2023  
Time: 2:30 pm – 4:00 pm

**ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)**  
ORGANISATION OF ISLAMIC COOPERATION (OIC)  
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Mid-Semester Examination  
Course Number: EEE 4385  
Course Title: Electrical and Electronic Technology

Summer Semester: 2022 – 2023  
Full Marks: 75  
Time: 90 Minutes

There are 05 (five) questions. Answer all 05 (five) questions. The symbols have their usual meanings. Marks of each question and corresponding CO and PO are written in the brackets.

1. Define Ohm's law. Find  $I_o$  in the circuit in Figure 1 by applying Ohm's law, Kirchhoff's voltage law (KVL) and Kirchhoff's current law (KCL). (15)

(CO1)  
(CO2)  
(PO2)

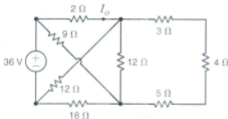


Figure 1

2. Define super nodes. Use nodal analysis to find  $V_o$  in the circuit in Figure 2. (15)

(CO1)  
(CO2)  
(PO2)

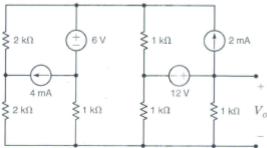


Figure 2

3. Using mesh analysis to evaluate the current  $I_0$  in the circuit in Figure 3.

(15)  
(CO2)  
(PO2)

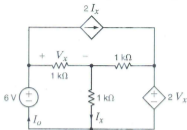


Figure 3

4. Define source transformation. Find  $V_0$  in the network in Figure 4 using superposition principle.

(15)  
(CO1)  
(CO2)  
(PO2)

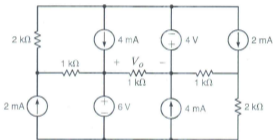


Figure 4

5. Define Norton's theorem. Find the value of  $R_L$  in Figure 5 for maximum power transfer. In addition, calculate the power dissipated in  $R_L$  under these conditions.

(15)  
(CO1)  
(CO2)  
(PO2)

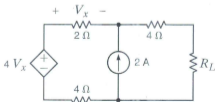


Figure 5