



ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)  
ORGANISATION OF ISLAMIC COOPERATION (OIC)  
**DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING**

Mid-Semester Examination

Course No.: Phy 4143

Course Title: Physics II

Winter Semester, A. Y. 2022-2023

Time: 90 Minutes

Full Marks: 75

There are 3 (**three**) questions. Answer all 3 (**three**) questions. The symbols have their usual meanings. Programmable calculators are not allowed. Marks of each question and corresponding COs and POs are written in the brackets.

1. a) Explain the difference between independent source and dependent source. Write down the names of the four different types of dependent sources and sketch their corresponding symbols. 5  
(CO1, PO1)

- b) Find  $V_o$  and the power absorbed by each element in the circuit of Fig. 1(b). 10  
(CO2, PO2)

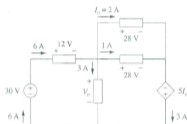


Fig. 1(b)

- c) Determine equivalent resistance  $R_{ab}$  in the circuit of Fig. 1(c). 10  
(CO2, PO2)

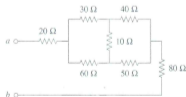


Fig. 1(c)

2. a) If the circuit shown in Fig. 2(a) has  $b$  branches,  $n$  nodes, and  $l$  independent loops, then determine the values of  $b$ ,  $n$ , and  $l$ . Verify that, these values satisfy the fundamental theorem of network topology:  $b = l + n - 1$ .

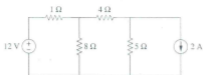


Fig. 2(a)

- b) Find  $v_0$  in the circuit in Fig. 2(b) and the power absorbed by the dependent source. (For solving the circuit, any method can be used)



Fig. 2(b)

- c) For the circuit in Fig. 2(c), find  $v_1$ ,  $v_2$ , and  $v_3$  using nodal analysis.

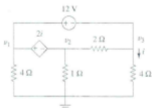


Fig. 2(c)

3. a) Calculate the voltages at the three non-reference nodes in the circuit of Fig. 3(a) using nodal analysis.

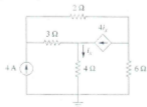


Fig. 3(a)

- b) Find  $i_o$  for the circuit in Fig. 3(b) using mesh analysis.

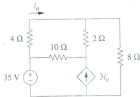


Fig. 3(b)

- c) Using mesh analysis, determine the value of current  $i_o$  in the circuit of Fig. 3(c).

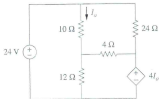


Fig. 3(c)