

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)  
ORGANISATION OF ISLAMIC COOPERATION (OIC)  
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Semester Final Examination  
Course No.: EEE 4307  
Course Title: Digital Electronics

Winter Semester, A. Y. 2022-2023  
Time: 3 Hours  
Full Marks: 150

There are 6 (six) questions. Answer all 6 (six) questions. The symbols have their usual meanings. Programmable calculators are not allowed. Marks of each question and corresponding COs and POs are written in the brackets.

1. a) Using  $r$ 's complement, ( $r$  represents the base) perform the subtraction operations: 12  
(i)  $(46894)_{10} - (1883)_{10}$ , (ii)  $(01100101)_2 - (11101000)_2$ . (CO2, PO2)
- b) Prove the identity of each of the following Boolean equations, using algebraic manipulation: 13  
(i)  $ABC\bar{C} + B\bar{C}D + BC + \bar{C}D = B + \bar{C}D$  (CO2, PO2)  
(ii)  $\bar{A}(A+B) + (B+A)(A+\bar{B}) = A+B$
2. a) Design a Full-Adder using two-level NAND gates. 8  
(CO2, PO2)
- b) Design an adder that is capable to add four following 4-bit binary numbers  $A = A_3A_2A_1A_0$ ,  $B = B_3B_2B_1B_0$ ,  $C = C_3C_2C_1C_0$  and  $D = D_3D_2D_1D_0$ . 10  
*Hint: You may use the Full-Adder Block that you have designed in question 2(a).* (CO3, PO2)
- c) Deduce the simplified expression of the following Boolean function using Karnaugh-Map in SOP form: 7  
 $F = (B+C+D)(A+B+\bar{C}+D)(\bar{A}+B+C+\bar{D})(A+\bar{B}+C+D)(\bar{A}+\bar{B}+C+D)$ . (CO2, PO2)
3. a) Determine the state table and the state diagram of the sequential circuit shown in Figure 3.a. 13  
(CO2, PO1)

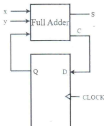


Figure 3.a

- b) Suppose you are given a supply of a 25 KHz square wave signal. Design a circuit that will take the mentioned square wave signal as input and give 12.5 KHz signal with 25% duty cycle as output. 12  
(CO3,  
PO2)

4. a) Show the logic diagram of a single bit memory cell using J-K flip flop. 8  
(CO1,  
PO1)
- b) The following memory units are specified by the number of words times the number of bits per word. Calculate the number of address lines and input-output data lines that are needed in each case: 12  
(CO2,  
PO2)
- i.  $2\text{ K} \times 16$
  - ii.  $64\text{ K} \times 8$
  - iii.  $16\text{ M} \times 32$
  - iv.  $96\text{ K} \times 12$
- c) Calculate the number of  $128\text{ K} \times 16$  RAM chips needed to provide a memory capacity of 2MB. Show necessary calculations. 5  
(CO2,  
PO2)

5. a) Design a sequence detector that has a form shown in figure 5.a. The output Z should be 1 if the input sequence ends in either 1000 or 0011 and Z should be 0 otherwise. 12  
(CO3,  
PO2)

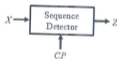


Figure 5.a

- b) Show the implementation of the following logic expression using CMOS. 13  
(CO2,  
PO2)
- $$F = A.B.C + B.(A + C)$$

6. a) Construct a J-K flip-flop with 'Preset' and 'Clear' inputs. Show the characteristic table.
- b) For the J-K flip-flops with inputs as shown in the Figure 6.b, sketch the time-line diagram for the  $Q_0$  and  $Q_1$  output relative to the clock pulse (CP).

10  
(CO1,  
PO1)  
15  
(CO2,  
PO2)

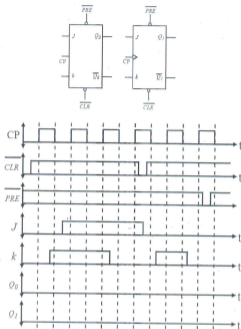


Figure 6.b