

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)  
ORGANISATION OF ISLAMIC COOPERATION (OIC)  
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

30

Semester Final Examination  
Course No.: EEE 4761  
Course Title: VLSI Circuits-I

Winter Semester, A. Y. 2022-2023  
Time: 180 Minutes  
Full Marks: 150

There are 6 (six) questions. Answer all 6 (six) questions. The symbols have their usual meanings. Programmable calculators are not allowed. Marks of each question and corresponding COs and POs are written in the brackets.

1. a) Explain symbols, different colors, and lines used to draw stick diagram. 10  
(CO2, PO2)
- b) Sketch the transistor-level circuit, and corresponding stick diagram of a given function of static CMOS:  $F = \overline{A \cdot B + C \cdot D}$ . 15  
(CO2, PO2)
2. a) For the given function,  $F = \overline{A}BC + A\overline{B}C + A\overline{B}\overline{C}$ , determine the truth table, and if each of the gate is implemented as CMOS gate, determine the number of transistors needed to build this logic. 10  
(CO3, PO4)
- b) Discuss raising and falling time asymmetry in complex combinational logic. From the below 3-input NAND logic circuit (Figure 1), determine the origin of such asymmetry and the ways to control using progressive sizing technique. 15  
(CO3, PO5)

 


Figure 1: NAND logic circuit with three inputs.

3. a) Explain what shift register (SR) is and two basic operations. Explain the synchronous and asynchronous data loading in shift register. 10  
(CO4, PO3)
- b) Design a 4-bits parallel in serial out (PISO) shift register (SR) as shown in Figure 2 using synchronous data loading. (Hint) Use AND/OR logic combination for data loading in SR. 15  
(CO4, PO5)

 


Figure 2: Logic symbol for 4-bits PISO SR.

4. a) Illustrate FPGA logic and explain how it differs from CPLD. Discuss two main categories of FPGA in terms of fabrication. Discuss a simplified building block of FPGA and one representative lookup table. 10  
(CO5, PO3)
- b) The PLA circuit shown below (Figure 3) is used to implement read only memory. Write the truth table and logic equations of F1, F2, F3, F4, and F5. 15  
(CO5, PO5)

 


Figure 3: Programmable logical array (PLA) circuit.

5. a) Discuss content addressable memory (CAM) and explain the differences with random access memory (RAM) technology. 10  
(CO6, PO3)
- b) Sketch a 3-input 4-output read only memory (ROM) (8x4 ROM) circuit that implements the following Boolean functions: 15  
(CO6, PO5)

$$A(x, y, z) = \Sigma(0, 1, 4, 7)$$

$$B(x, y, z) = \Sigma(1, 3, 6, 7)$$

$$C(x, y, z) = \Sigma(2, 5)$$

$$D(x, y, z) = \Sigma(0, 1, 2, 4, 5, 7)$$

6. a) Discuss the key differences between BiCMOS and CMOS technology in brief. Explain the operation of a BiCMOS two input NAND gate with the help of a circuit diagram. 10  
(CO7, PO4)
- b) The VTC curve of BiCMOS inverter in Figure 4 shows smaller  $V_{OUT}$  at low input ( $V_{IN}$ ), and comparatively higher (non-zero)  $V_{OUT}$  at higher  $V_{IN}$  signal as compared to conventional CMOS technology. Explain the origin of such behavior. 15  
(CO7, PO5)

 


Figure 4: Comparison of VTC characteristics of CMOS and BiCMOS circuit.