

3

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)
ORGANISATION OF ISLAMIC COOPERATION (OIC)
DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Final-Semester Examination
Course No.: PHY 4241
Course Title: Physics II

Summer Semester, A. Y. 2022-2023
Time: 3 hours
Full Marks: 150

There are 6 (six) questions. Answer all 6 (six) questions. The symbols have their usual meanings. Programmable calculators are not allowed. Marks of each question and corresponding COs and POs are written in the brackets.

1. a) Explain why capacitors and inductors are called storage elements.

13
(CO2,
PO2)

The voltage across a 200-mH inductor is given by

$$v(t) = 3t^2 + 2t + 4 \text{ V for } t > 0.$$

Determine the current $i(t)$ through the inductor. Assume that $i(0) = 1 \text{ A}$.

- b) Calculate the equivalent inductance for the inductive ladder network in Figure 1b.

12
(CO2,
PO2)



Figure 1b

2. a) An initially uncharged 1-mF capacitor has the current shown in Figure 2a across it. Calculate the voltage across it at $t = 2 \text{ ms}$ and $t = 5 \text{ ms}$.

12
(CO2,
PO2)

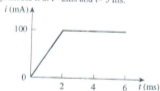


Figure 2a

- b) Determine v_C , i_L , and the energy stored in the capacitor and inductor for the circuit shown in Figure 2b under dc conditions.

13
(CO2,
PO2)



Figure 2b

3. a) Find the value of R_L for maximum power transfer in the circuit shown in Figure 3a.

20
(CO2,
PO2)

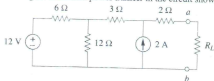


Figure 3a

- b) Find the maximum power transfer that takes place in the circuit shown in Figure 3a.

05
(CO2,
PO2)

4. Find I_o in the circuit shown in Figure 4 using superposition.

25
(CO2,
PO2)

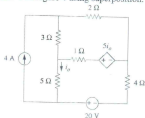


Figure 4

- 5 a) Find the amplitude, phase, period, and frequency of the following sinusoids

i) $v(t) = 12 \cos(50t + 10^\circ)$

ii) $30 \sin(4\pi t - 75^\circ)$

10
(CO2,
PO2)

- b) Determine the input impedance of the circuit shown in Figure 5b at an angular frequency of 10 rad/s.

15
(CO2,
PO2)



Figure 5b

- 6 Find current I in the circuit shown in Figure 6.

25
(CO2,
PO2)

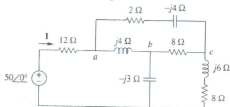


Figure 6