

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)
ORGANISATION OF ISLAMIC COOPERATION (OIC)

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Semester Final Examination

Summer Semester, A. Y. 2022-2023

Course No.: EEE 6295

Time: 3 Hours

Course Title: Advanced Electronics

Full Marks: 150

There are **8 (eight)** questions. Answer **any 6 (six)** questions. All questions carry equal marks. Marks in the margin indicate full marks. Programmable calculators are not allowed. Do not write on this question paper.

1. a) An instrumentation amplifier shown in Fig. 1.a is an amplifier of low-level signals used in process control or measurement applications and commercially available in single-package units. Show that

15

$$v_o = \frac{R_2}{R_1} \left(1 + \frac{2R_3}{R_4} \right) v_2 - v_1.$$

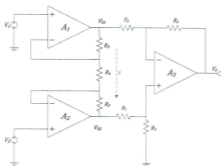


Fig. 1.a

- b) Design an operational amplifier circuit with inputs v_1 and v_2 such that $v_o = 20v_1 - 12v_2$. Use only one op-amp in the design.

10

2. Draw the circuit diagram and derive the output for the following circuits considering ideal operational amplifier.

5x5= 25

- Voltage follower circuit,
- Summing amplifier circuit,
- Inverting amplifier circuit,
- Differentiator circuit and
- Integrator circuit.

3. a) The digital-to-analog converter (DAC) transforms digital signals into analog form. A typical example of a four-bit DAC is illustrated in Fig. 3.a. Now, in the op-amp circuit of Fig. 3.a, let $R_f = 10k\Omega$, $R_1 = 10k\Omega$, $R_2 = 20k\Omega$, $R_3 = 40k\Omega$, and $R_4 = 80k\Omega$. Obtain the analog output for binary inputs [0000], [0001], [0010], ..., [1111].

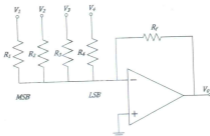


Fig. 3.a

- b) Construct a one-shot multivibrator circuit. 5
4. Draw the circuit diagram, input-output relation with time, and transfer function for the following detector circuits. 5×5= 25
- Non-inverting zero-crossing detector,
 - Inverting zero-crossing detector,
 - Unipolar Triangular wave generator,
 - Third order high pass filter and
 - Non-inverting negative level detector.
5. a) Draw a square wave generator circuit when the input is a triangular wave and discuss its input-output relation with time. Calculate the upper and lower threshold of the circuit. 15
- b) Design an operational amplifier circuit with inputs v_1 , v_2 , v_3 and v_4 such that output is $v_0 = 3v_1 + 5v_2 - 10v_3 - 20\frac{dv_4}{dx}$. 10
6. a) Discuss the operation of a free running multi-vibrator circuit with the help of a diagram. Derive the equation for the time period (T). 15
- b) Design an astable multi-vibrator circuit to generate a square wave with 1 kHz frequency (f). 10
7. a) What is a passive filter? Draw a passive low-pass and analyze its output relation with frequency. Discuss its disadvantages. 15
- b) Draw an active high-pass and low-pass filter and find their gains. 10
8. a) Draw an active band-reject filter and find its gain, quality factor. 10
- b) Design an active bandpass voice filter that has lower and upper cutoff frequencies of 500 Hz and 5 kHz respectively. Use first order low pass and high pass filter. Draw the circuit diagram of your design. 15