

ISLAMIC UNIVERSITY OF TECHNOLOGY (IUT)  
THE ORGANISATION OF THE ISLAMIC CONFERENCE (OIC)


DEPARTEMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING

Semester Final Examination  
Course No.: EEE 6801  
Course Title: Power Electronics


Summer Semester. A.Yr. 2022-2023  
Time: 3 hours  
Full Marks: 150

There are 8 questions. Answer any 6 questions. All questions carry equal marks.

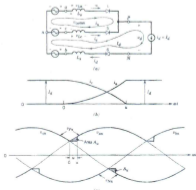
- 1.(a) Draw the circuit diagram of a three phase uncontrolled rectifier with resistive load. Explain why this rectifier is known as six pulse type. Drawing the output voltage wave shapes, find the expression of average output voltage.
- (b) For the three phase rectifier with a purely resistive load, find the efficiency, FF, RF, TUF and PIV of each diode if the delivers a dc current of 60 A, average voltage 280.7 V with a source frequency of 50 Hz.
- 2.(a) The following figure shows the current commutation process of a three-phase uncontrolled rectifier with the highly inductive load. Derive the expression of  $A_{\omega}$ , commutation angle  $\mu$  and average output voltage  $V_d$  for this converter.



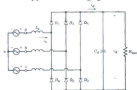- (b) For the following circuit, assume the ac-side inductance  $L_S$  to be negligible. Instead, an inductor  $L_d$  is placed between the rectifier output and the filter capacitor. Derive the minimum value of  $L_d$  in terms of  $V_{LL}$ ,  $\omega$ , and  $I_d$  that will result in continuous  $i_d$ , assuming that the ripple in  $v_d$  is negligible.




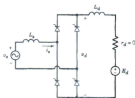3. (a) Following is a circuit diagram of a practical single phase controlled rectifier.



Draw the wave shapes of  $v_d$  and  $i_d$  with  $v_s$  for continuous  $i_d$  of this converter. Also derive the expression of the average output voltage  $V_d$ .

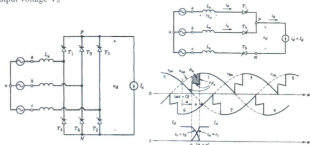- (b) From the following diagrams, find the expressions of commutation angle  $\mu$  and average output voltage  $V_d$



4.(a) Draw the circuit diagram of a buck converter. Plot the inductor current  $i_L$ , inductor voltage  $v_L$  on the same scale for boundary between continuous and discontinuous conduction of  $i_L$ . Derive the expressions of inductor current  $I_{LB}$  and output current  $I_{OB}$  at the boundary conditions. Derive the expressions of inductor current and duty cycle for this discontinuous mode of operation.

(b) With the circuit diagram of a boost converter. Plot the inductor current  $i_L$ , inductor voltage  $v_L$  on the same scale for boundary between continuous and discontinuous conduction of  $i_L$ . Derive the expressions of inductor current  $I_{LB}$  and output current  $I_{OB}$  at the boundary conditions. Derive the expressions of inductor current and duty cycle for this discontinuous mode of operation.

5. (a) For a buck-boost converter operating in discontinuous mode, the expression of  $D$  is given by

$$D = \frac{V_o}{V_s} \sqrt{\frac{L_o}{I_{oB,max}}}$$

Plot the converter characteristics that is draw  $D$  versus  $(I_o/I_{oB,max})$  with  $V_o$  constant identify discontinuous and continuous mode of conduction.

(b) Draw the circuit diagram of a CUK converter. Explain the operation of the converter with proper derivations.

6.(a) In a Cuk converter operating at 50 kHz,  $L_1=L_2=1$  mH and  $C_1=5$   $\mu$ F. The output capacitance is sufficiently large to yield an essentially constant output voltage. Here  $V_d=10$  V and the output  $V_o$  is regulated to be constant at 5 V. It is supplying 5 W to a load. Assume ideal components. Calculate the percentage errors assuming constant voltage across  $C_1$  or assuming constant currents  $i_{L1}$  and  $i_{L2}$ .

(b) For a three phase 50 Hz inverter, sketch the gating signals for 120 degree conduction and find the expressions of line to line voltage. If a Y load of  $R=10$  ohm, and  $L=10$  mH per phase is connected to this inverter, calculate the line currents.

7. (a) Provide some practical applications of SMPS. For LED lamps, which converter is being used. Propose a new topology that may improve the performance of the converter.

(b) Why discontinuous mode of operation could provide better performance for a de-dc converter? Find the expression of output voltage of a boost type converter.

8. (a) Describe the importance of the application of inverters with the context of using these in renewable energy systems. Draw a block diagram comprising all possible connection of converters to obtain a sustainable energy system. Describe the function of each converter in the block diagram.

(b) Write down the various advanced modulation techniques used in inverter operations. Explain any method that can be effectively used to reduce the unwanted harmonics at the output of an inverter.